



# 3055 BA SANGAM COLLEGE

PH: 6674003/9264117 E-mail: basangam@connect.com.fj



WEEK 11

SCHOOL: BA SANGAM COLLEGE  
SUBJECT: PHYSICS


YEAR: 13  
NAME OF STUDENT: \_\_\_\_\_

STRAND	4- ELECTROSTATIC
SUB-STRAND	Capacitors in a circuit
LEARNING OUTCOME	<ul style="list-style-type: none"> <li>To understand about capacitors connected in circuits</li> </ul>

## Capacitors in a circuit
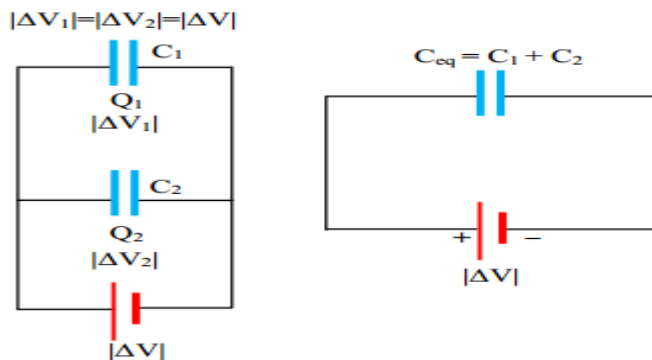
### Capacitors in Parallel

- we have two capacitors  $C_1$  with charge  $Q_1$  and  $C_2$  with charge  $Q_2$  that are connected in parallel



- total capacitance of the circuit can be found by


$$C_{eq} = C_1 + C_2 + C_3 + C_4 + \dots$$

### Rule

- The equivalent capacitance is the sum for all the capacitors.
- The voltage across each capacitor is the same.
- The charge in each capacitor is different; depending on the capacitor values.
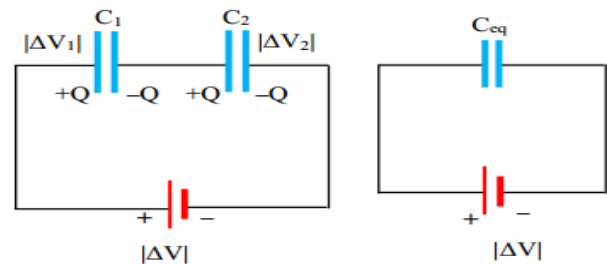
### Capacitors in Series

Suppose two initially uncharged capacitors  $C_1$  and  $C_2$  are connected in series as shown



- the generalisation to any number of capacitors in series is:


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} + \dots$$

### Rule

- The equivalent capacitance is the inverted sum of the reciprocals of all the capacitors.
- The voltage across each capacitor is different; depending on the capacitor values.
- The charge across each capacitor is the same.
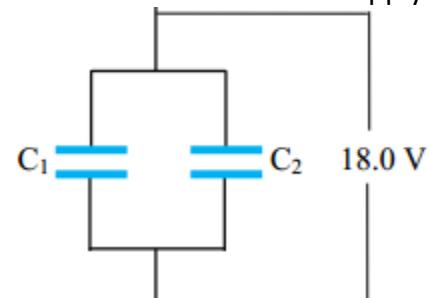
### Example (parallel circuit)

Shown below are two capacitors ( $C_1 = 3 \mu\text{F}$ ,  $C_2 = 6 \mu\text{F}$ ) are connected to a 18.0 V supply.




- Determine the equivalent capacitance of the combination
- What is the total charge flowing in the circuit.
- Determine the voltage across C2.
- Determine the charge across C2.
- Calculate the energy stored in C2.

**Solution**

- $C_{eq} = C_1 + C_2 = 3\mu\text{F} + 6\mu\text{F} = 9\mu\text{F}$
- $Q = C\Delta V = (9 \times 10^{-6}) \times (18.0) = 1.62 \times 10^{-4} \text{ C} = 0.162 \text{ mC}$
- Since it's a parallel combination the voltage will be same in both the  $\Delta V = 18.0 \text{ V}$ .
- $Q_2 = C_2 \Delta V = (6 \times 10^{-6})(18.0) = 1.08 \times 10^{-4} \text{ C}$   
 $Q_1 = C_1 \Delta V = (3 \times 10^{-6})(18.0) = 0.54 \times 10^{-4} \text{ C}$   
 $Q_T = Q_1 + Q_2 = 0.108 \text{ mC} + 0.054 \text{ mC} = 0.162 \text{ mC}$
- $E_2 = \frac{1}{2} C_2 V^2 = \frac{1}{2} (6 \times 10^{-6})(18.0)^2 = 9.72 \times 10^{-4} \text{ J}$  OR  
 $E_2 = \frac{1}{2} Q_2 V = \frac{1}{2} (1.08 \times 10^{-4})(18.0) = 9.72 \times 10^{-4} \text{ J}$  OR

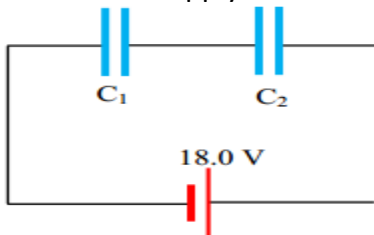**Example (series circuit)**

Shown below is two capacitors ( $C_1 = 3\mu\text{F}$ ,  $C_2 = 6\mu\text{F}$ ) connected to a 18.0 V supply.



- Determine the equivalent capacitance of the combination
- What is the total charge flowing in the circuit.
- Determine the voltage across C2.
- Determine the charge across C2.
- Calculate the energy stored in C2.

- $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{3\mu\text{F}} + \frac{1}{6\mu\text{F}} = \frac{1}{2\mu\text{F}}$   
 $C_{eq} = 2\mu\text{F}$
- $Q = C\Delta V = (2 \times 10^{-6}) \times (18.0) = 3.6 \times 10^{-5} \text{ C} = 0.036 \text{ mC}$
- $\Delta V_2 = \frac{Q_T}{C_2} = \frac{3.6 \times 10^{-5}}{6 \times 10^{-6}} = 6 \text{ V}$
- The charge across each capacitor is the same;  
 $\therefore Q_T = Q_2 = 3.6 \times 10^{-5} \text{ C} = 0.036 \text{ mC}$
- $E_2 = \frac{1}{2} C_2 V^2 = \frac{1}{2} (6 \times 10^{-6})(6.0)^2 = 1.08 \times 10^{-4} \text{ J}$  OR  
 $E_2 = \frac{1}{2} Q_2 V = \frac{1}{2} (3.6 \times 10^{-5})(18.0) = 1.08 \times 10^{-4} \text{ J}$  OR  
 $E_2 = \frac{(Q^2)}{2C_2} = \frac{(3.6 \times 10^{-5})^2}{2 \times (6 \times 10^{-6})} = 1.08 \times 10^{-4} \text{ J}$

**EXERCISE**

- A 2 pF and 6 pF capacitors are connected to a 120 V power supply in parallel. Calculate:
  - total equivalent capacitance of the circuit. (1mark)
  - the total charge coming out of the power supply. (1mark)
  - the charge on each capacitor. (2marks)
- A 5  $\mu\text{F}$  and 7  $\mu\text{F}$  capacitors are connected to a 24 V power supply in Series. Calculate:
  - total equivalent capacitance of the circuit. (2marks)
  - the total charge coming out of the power supply. (1mark)
  - the charge on each capacitor. (1mark)
  - Voltage across each capacitor (2marks)