



# 3055 BA SANGAM COLLEGE

PH: 6674003/9264117 E-mail: basangam@connect.com.fj



## WORKSHEET 16

SCHOOL: BA SANGAM COLLEGE

YEAR: 13

SUBJECT: PHYSICS

NAME OF STUDENT: \_\_\_\_\_

STRAND	5 - DIRECT CURRENT
SUB-STRAND	5.2 – Kirchoff's Laws
LEARNING OUTCOME	To study about more complex circuits using Kirchoff's Laws


Simple circuits are analysed using Ohm's law. More complex circuits containing several sources of *emf* and

### Kirchoff's Rule 1- The junction rule


*"The sum of currents entering any junction must be equal to the sum of the currents leaving that junction."*

$$I_{\text{entering}} = I_{\text{leaving}}$$

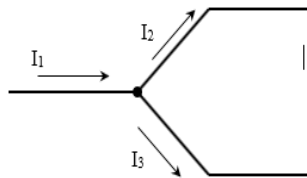This junction rule is based on the **conservation of charge**.



(a) Schematic diagram

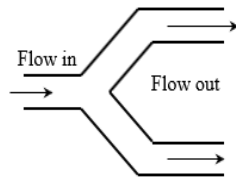


(b) A mechanical analogue

If we apply the junction rule to the above schematic diagram, we get

$$I_{\text{entering}} = I_{\text{leaving}} \rightarrow I_1 = I_2 + I_3.$$

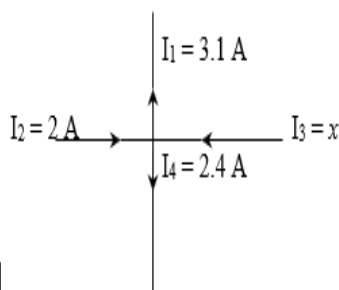Example.

Calculate the unknown current in the circuit given.



Using the junction rule, we get

$$I_2 + I_3 = I_1 + I_4$$

$$x = I_1 + I_4 - I_2$$


$$x = (3.1 + 2.4 - 2) \text{ A}$$

$$x = 3.5 \text{ A}$$

Kirchoff's rule 2. The loop rule - *"The sum of the potential differences across all elements around any closed-circuit loop must be zero."*

- The loop rule is based on the principle of **conservation of energy**.


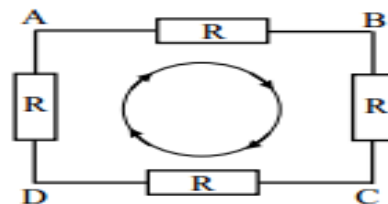
-Any charge moving around any closed loop in a circuit must gain as much energy as it loses.




$$V_{AB} + V_{BC} + V_{CD} + V_{DA} = 0$$

### Problem solving strategy.

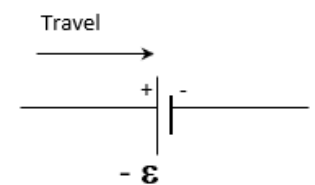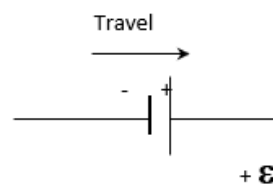1. Choose a junction and use the first rule to relate all the currents.
2. Choose any closed loop in the network and designate a direction (clockwise or counter clockwise).
3. For *emf*'s (voltage) use the following rules:



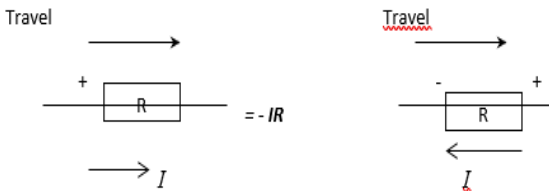
resistances are analysed using Kirchoff's laws.



4. Solve the equations simultaneously for the unknown quantities.

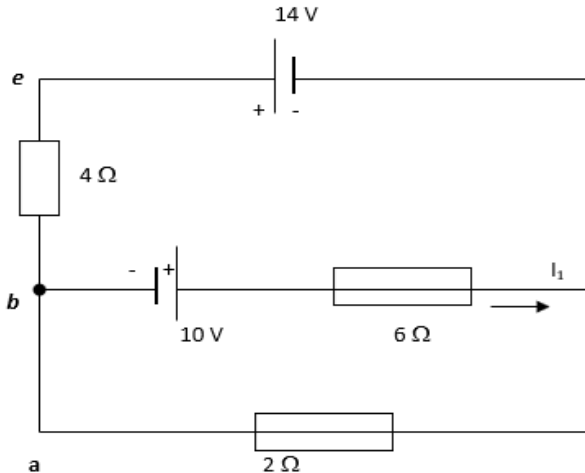**Example**

Find the currents  $I_1$ ,  $I_2$  and  $I_3$  in the multi-loop circuit given.



**SOLUTION**

**Step 1.** Choosing junction  $c$  and applying the Kirchoff's first rule we get  $I_1 + I_2 = I_3$ . eq (1)

**Step 2.** The circuit has three loops but only two is needed, so let's take loops  $abcd$  and  $befcb$  and traverse in a clockwise direction

Loop  $abcd$ :  $10\text{ V} - 6 I_1 - 2 I_3 = 0$

Loop  $befcb$ :  $-14\text{ V} + 6 I_1 - 10\text{ V} - 4 I_2 = 0$

Loop  $befcb$  simplifies to  $-24\text{ V} + 6 I_1 - 4 I_2 = 0$

**Step 3-**We now have to use the equations 1, 2 and 3 and solve them simultaneously. Take equation 1 and substitute in equation 2.

$$10 - 6 I_1 - 2 (I_1 + I_2) = 0$$

**Step 4.** We have to use the equations (3) and (4) and eliminate one of the variables.

Take equation (3) and divide throughout by 2.

$$12 - 3 I_1 + 2 I_2 = 0 \quad \text{eq- (5)}$$

**Step 5.** Add equation (5) to (4) to eliminate  $I_2$ , gives

$$12 - 3 I_1 + 2 I_2 = 0$$

$$(+)\quad 10 - 8 I_1 - 2 I_2 = 0$$

$$\underline{22 - (11) I_1 = 0} \quad (11) \quad I_1 = 2 \text{ A} \quad \underline{I_1 = 2 \text{ A}}$$

**Step 6.** Substituting  $I_1$  in (5) results in a value for  $I_2$

$$12 - 3 (2) + 2 I_2 = 0, \quad I_2 = \underline{-3 \text{ A}}$$

Step vii. Finally use equation (1) to calculate  $I_3$

$$I_3 = I_1 + I_2, \quad I_3 = \underline{-1 \text{ A}}$$

The values for the currents are:


$$I_1 = \underline{2 \text{ A}} \quad I_2 = \underline{-3 \text{ A}} \quad I_3 = \underline{-1 \text{ A}}$$

-The **negative** values of  $I_2$  and  $I_3$  indicate that the directions of the currents are **opposite** to that designated initially.

**EXERCISE**

Use the circuit in Figure 5.17 to answer the questions that follow.

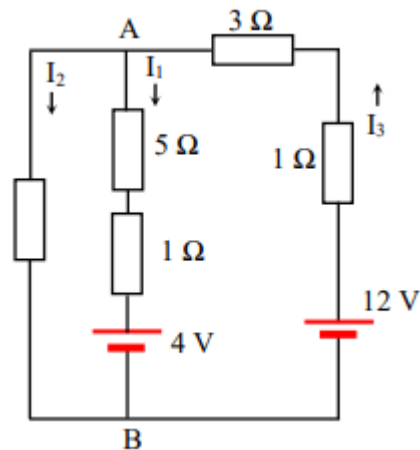- i. Calculate the values of  $I_1$ ,  $I_2$  and  $I_3$ .
- ii. Find the potential difference between Points A and B.



**6 Marks**

