



3055 BA SANGAM COLLEGE

PH: 6674003/9264117 E-mail: basangam@connect.com.fj



WORKSHEET 17

SCHOOL: BA SANGAM COLLEGE

YEAR: 13

SUBJECT: PHYSICS


NAME OF STUDENT: _____

STRAND	5 - DIRECT CURRENT
SUB-STRAND	5.2 – The Wheat stone Bridge
LEARNING OUTCOME	To understand how a wheat stone bridge works

The Wheat stone Bridge

This is a special circuit that can be used to determine the resistance of an unknown resistor by comparison with three other resistances.

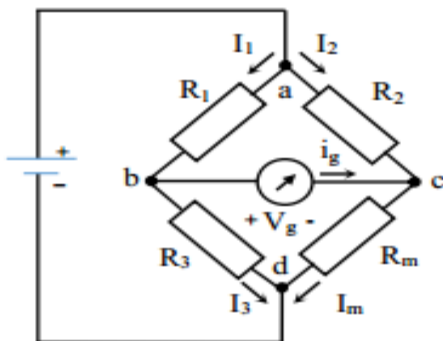The galvanometer is used to detect the condition $I_g = 0$. When the circuit satisfies the condition $I_g = 0$ we say that “the bridge is balanced”. It is always true that $V_g = 0$.



To find the value of the unknown resistor, use

$$\frac{R_3}{R_1} = \frac{R_m}{R_2}$$

$$R_m = \frac{R_3}{R_1} R_2$$

EXAMPLE

- 1) Consider using a Wheatstone bridge having $R_1 = 200 \Omega$ and $R_2 = 2000 \Omega$ to measure a resistance R_m . The bridge is balanced by adjusting R_3 until $R_3 = 250 \Omega$. What is the value of R_m ?

$$\frac{R_3}{R_1} = \frac{R_m}{R_2}$$

$$\frac{250}{200} = \frac{R_m}{2000}$$

$$R_m = \frac{250}{200}(2000)$$

$$R_m = 2500 \Omega \text{ or } 2.5 \text{ k}\Omega$$

- 2) In the Wheatstone bridge circuit shown in Figure 5.23, R_1 and R_2 are $200\ \Omega$ and $300\ \Omega$ resistors. R_m is a resistor of unknown resistance. The bridge is balanced when R_3 is set to $180\ \Omega$. Calculate the resistance of R_m .

$$R_1 = 200\ \Omega \quad R_2 = 300\ \Omega \quad R_3 = 180\ \Omega \quad R_m = ??$$

$$R_m = \frac{R_3}{R_1} R_2$$

$$R_m = \frac{180}{200} (300)$$

$$R_m = 270\ \Omega$$

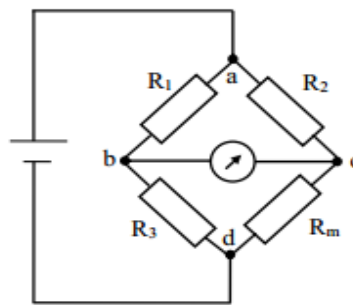


Figure 5.23

EXERCISE

- 1) Use the circuit in Figure 5.24 to answer the following questions.

- Name the circuit formed.
- What is current flowing in arm BD?
- State the two laws used to find the current in the different branches of this circuit.
- Calculate the value of unknown resistance.

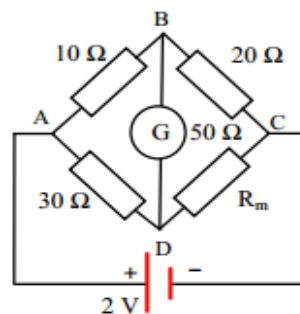


Figure 5.24

- 2) Figure 5.25 below shows a Wheatstone bridge connection between 'a' and 'b'. Calculate the value of X, if the bridge is balanced.

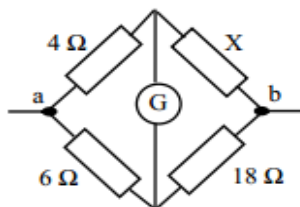


Figure 5.25

SOLUTION